

Lecture 4

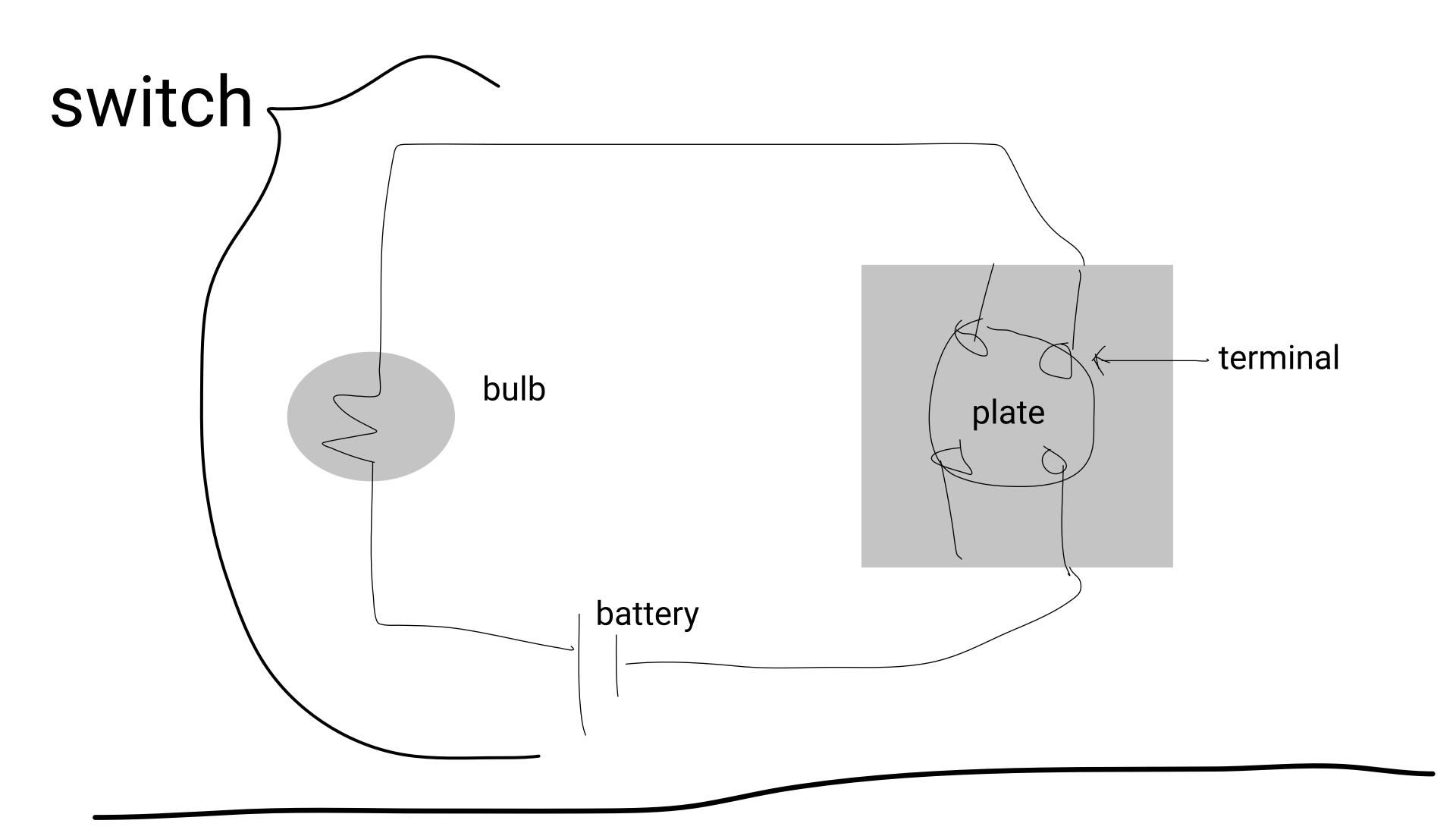


ACTIVE HIGH switch

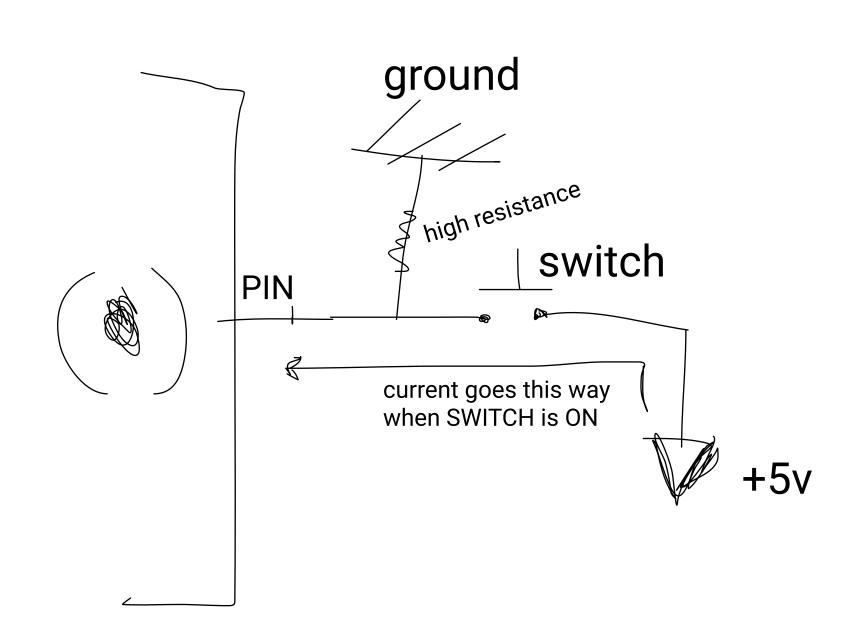

IDEAL CASE: current follow least resistive path

ACTIVE LOW switch

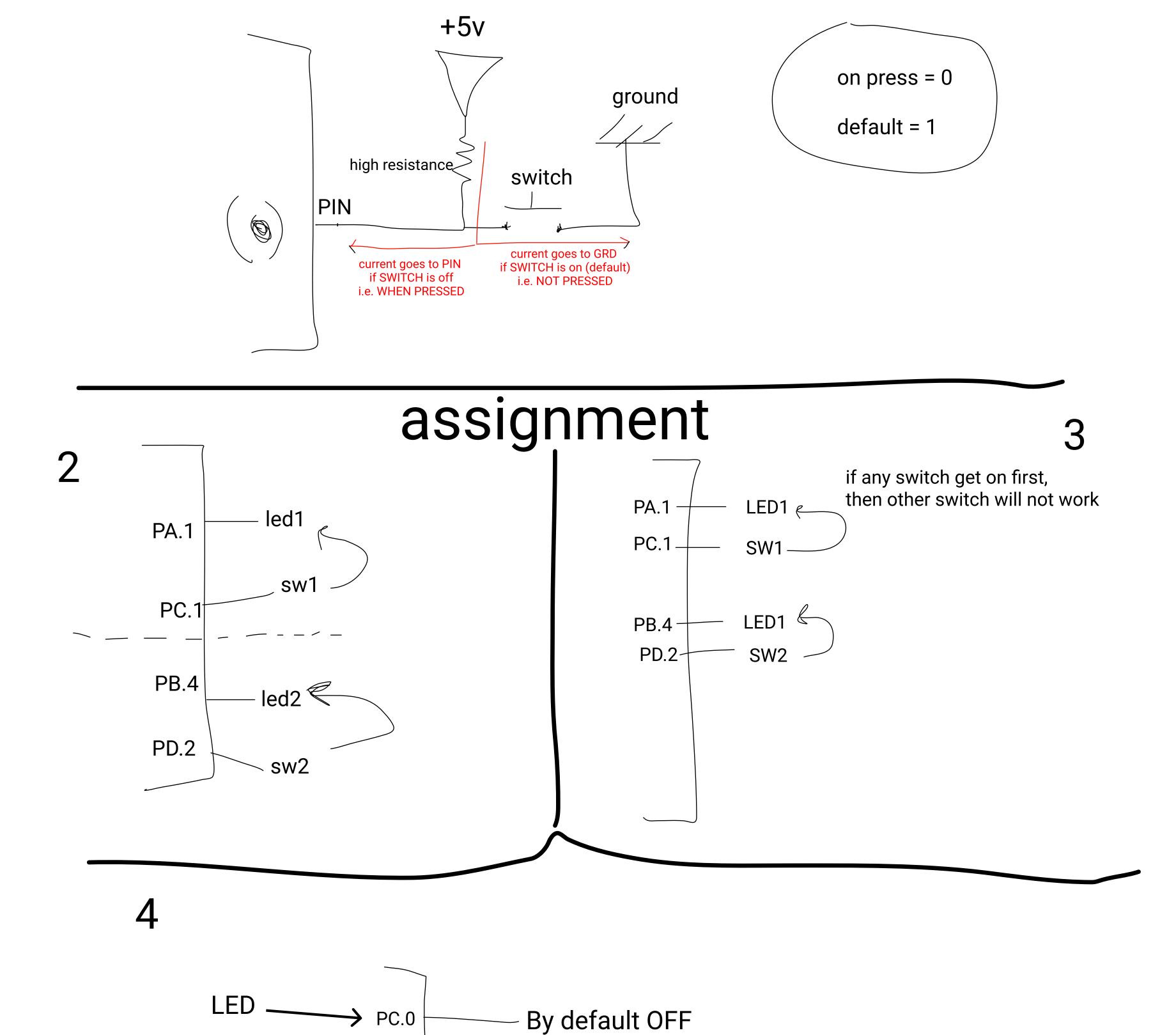

constant glow LED

blink LED

turn off LED

PC.2

SWITCHES