lecture 6

assignment 3

PC.0 -> MOTOR

PC.1 -> MOTOR

PC.2 -> LED


PD.0 -> counter +

PD.1 -> counter -

PD.2 -> START

PD.3 -> STOP/reset

ELEVATOR

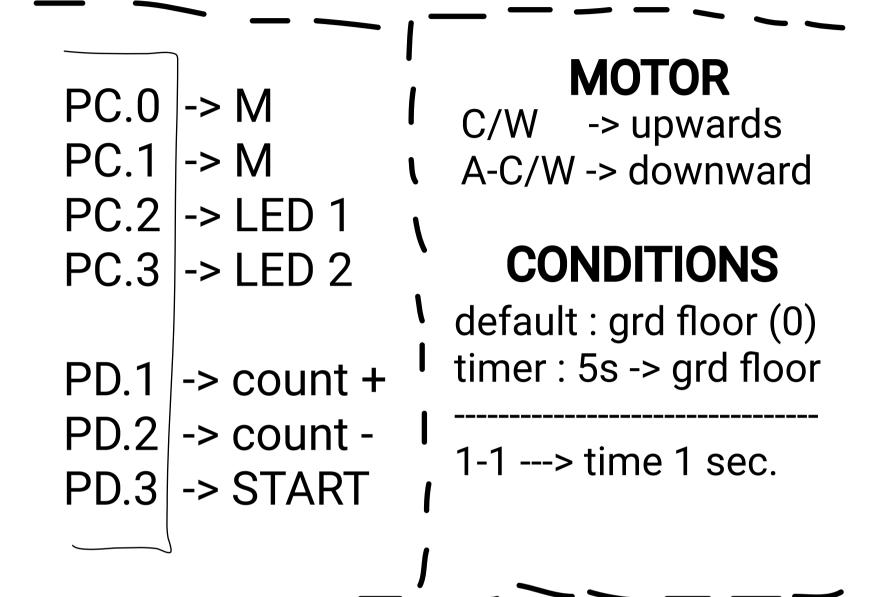

LCD

