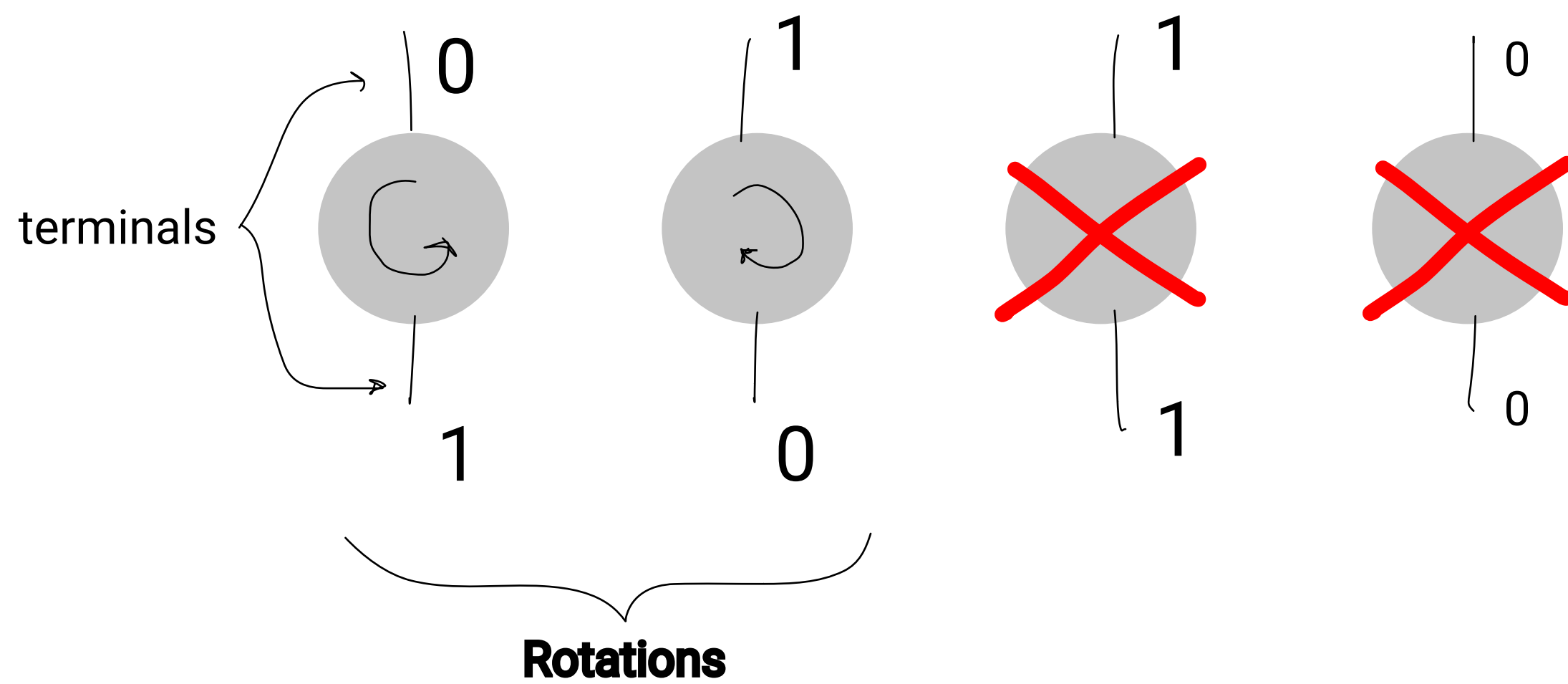


# Lecture 5


configurations : total 4

{ DC motor }



1

PC.0

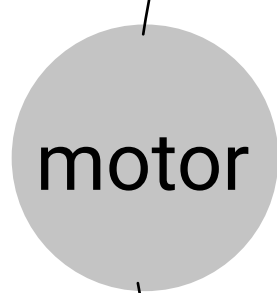

PC.1

switch 1

clock

switch 2


anti-clock

switch 3


stop

2

PC.2

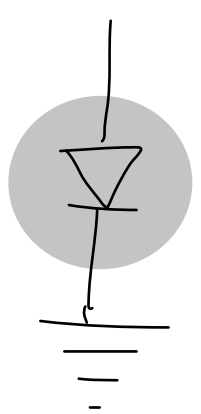

PC.0

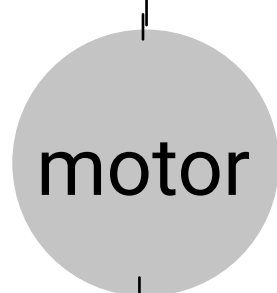

PC.1

switch 1

clock and LED blink

switch 2


anti-clock and LED glow

switch 3

stop

both

assignment

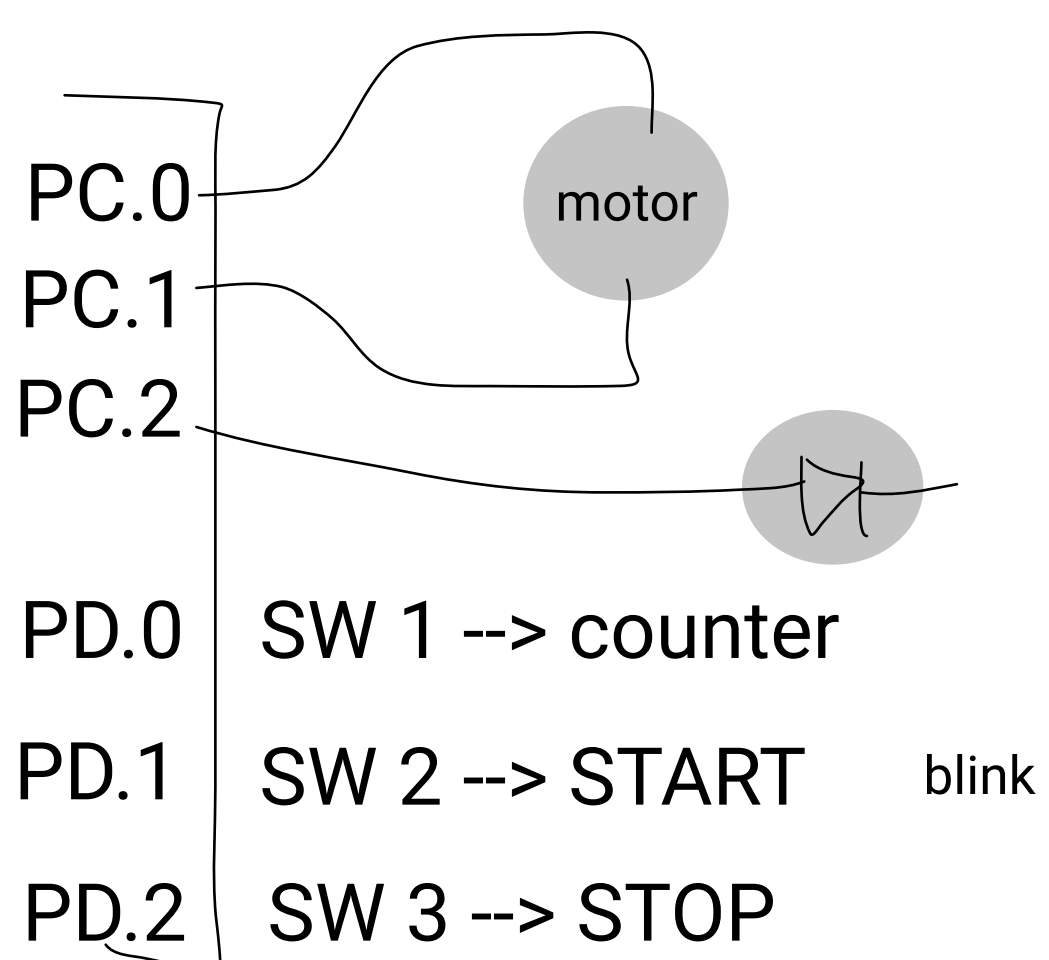

~ By K.S.